

Subject : Digital Electronics

DPP - 01

Chapter : Boolean Theorems and GATES

Topic : Boolean Theorems and Basics of Gates (Part-1)

[MCQ]

1. $(A + B)(A + C)(A + \bar{C})$ is equivalent to

- (a) $A + BC$ (b) $A + B\bar{C}$
(c) 0 (d) A

[MCQ]



2. A logical function is given as:

$$f(A, B, C) = B\bar{C}[A + B\bar{C}D + \bar{B}CD + \bar{A}B\bar{C} + \bar{A}\bar{B}\bar{C}]$$

is equivalent to

- (a) $\bar{A}\bar{B}CD$ (b) $B\bar{C}$
(c) $\bar{A}\bar{B} + B\bar{C} + CD$ (d) $AB\bar{C}D$

[NAT]



3. If we have 4-variables in a logical function, then number of non-dual logical functions possible ____.

[MCQ]



4. A logical function

 $f(A, B, C) = (A + B)(\bar{B} + C)(A + C)$, then \bar{f} will be equal to

- (a) $AB + \bar{B}C$ (b) $\bar{A}\bar{B} + B\bar{C}$
(c) $\bar{A}\bar{B} + \bar{A}\bar{C}$ (d) $AB + AC$

[MCQ]




5. Which of the following statement is true?

- (a) Dual function f^D is always equals to f .
(b) NAND is self dual in nature.
(c) NOT is self dual in nature.
(d) Number of self dual function with 3-variables is 8.

[MCQ]



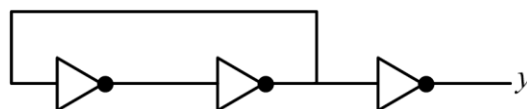6. A digital circuit is designed as shown:




This circuit works as

- (a) Astable multivibrator as odd number of Not gates are used.
(b) Bistable multivibrator
(c) Monostable multivibrator
(d) None of these

[NAT]



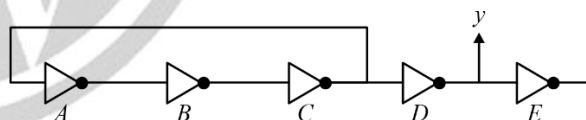7. An astable multivibrator circuit is designed as shown:



NOT gates A, B & C are of logic family TTL with delay $t_d = 20/3$ nsec of each gate and gates D & E are of logic family ECL with delay $t'_d = 10/3$ nsec of each gate, then frequency of the waveform at output y is _____ MHz.

[MCQ]

8. Logical function $f(A, B, C, D) = AB + \bar{A}CD + \bar{B}CD$ is equivalent to

- (a) $AB + \bar{B}C$
(b) $AB + CD$
(c) $\bar{A}C + \bar{B}C$
(d) $AB + \bar{B}C$

[MCQ]



9. A logical function is given as:

$$f(A, B, C) = \bar{A}\bar{B} + \bar{A}BC + \bar{A}\bar{B}\bar{C}$$


then which of the following statement is true?

- (a) $f(A, B, C) = \bar{A}\bar{B} + B\bar{C}$
- (b) $f(A, B, C) = \bar{A} + \bar{C}$
- (c) $f(A, B, C)$ is a self dual function.
- (d) None of the above

[MCQ]



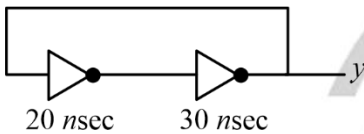10. A logical circuit is designed as shown:



Output y is

- (a) A bistable multivibrator's output
- (b) A square waveform with $f = 10$ MHz
- (c) A square waveform with $f = 25$ MHz
- (d) None of the above.

[MCQ]



11. Which of the following is true?

- (a) $\overline{\bar{A}B + A\bar{B}} = (\bar{A} + \bar{B})(A + B)$
- (b) $\overline{\bar{A}BCD} = \bar{A} + \bar{B} + \bar{C} + \bar{D}$
- (c) $\overline{\bar{A}\bar{B}.C} = (A + \bar{C})(\bar{B} + \bar{C})$
- (d) None of these

Answer Key

1. (d)
2. (b)
3. (65280)
4. (b)
5. (c)

6. (b)
7. (25)
8. (b)
9. (c)
10. (a)
11. (c)



Any issue with DPP, please report by clicking here:- <https://forms.gle/t2SzQVvQcs638c4r5>
For more questions, kindly visit the library section: Link for web: <https://smart.link/sdfez8ejd80if>



PW Mobile APP: <https://smart.link/7wwosivoicgd4>